



In class activity:

1. Draw a half adder using NAND gates.
2. Draw a full adder circuit using NAND gates.
3. Draw Half subtractor using NOR gates.
4. Draw block diagram of 3-8 decoder.
5. Design and draw a circuit diagram for 8x3 encoder (octal to binary encoder).
6. Draw block diagram of 1x4 Demultiplexer.