

Don't care conditions are used in Karnaugh maps (K-maps) when certain input combinations will never occur or their output doesn't matter in a digital system

1. you are designing a digital system to **encode a BCD (Binary Coded Decimal)** input. BCD only allows **decimal digits 0–9** , circuit takes a **4-bit BCD input (A, B, C, D)** and **outputs 1 if the number is less than or equal to 5, otherwise outputs 0.**
2. You are designing a control system for an elevator in a 3-floor building. The elevator has a 2-bit input to represent the current floor:  
Floor 0 → 00  
Floor 1 → 01  
Floor 2 → 10
3. You are designing a traffic light controller for a 3-way intersection. There are 3 sensors (inputs) that detect the presence of vehicles on each road:  
A – Sensor on Road A  
B – Sensor on Road B  
C – Sensor on Road C  
Each sensor outputs 1 if a vehicle is present and 0 if not.  
However, due to the layout of the intersection, certain sensor combinations are not physically possible. For example:  
All three roads cannot have cars at the same time (due to traffic flow restrictions).  
Also, no car at all (000) will turn the signal to flashing yellow, which is a separate case (not controlled here).