

---

---

# Computer Systems

Logic Expression Simplification

---

Part 02

---

---

# Single Gate Type Circuits






- Circuits are preferred to be built using a single gate type because it's cheaper.
- Manufacturing ICs with different types of gates are expensive.
- Therefore when we preparing the circuits we consider about Functional Completeness.

# Functional Completeness






- AND, OR and NOT operations are the primary functionalities.
- Therefore, any set of gates that can demonstrate all three functionalities is called Functionally Complete Set.
- Functionally Complete Sets
  - AND , OR and NOT
  - AND and NOT
  - OR and NOT
  - NAND
  - NOR

A set of Boolean operators, which can be used to express all possible truth tables by combining members of the set into a Boolean expression.
     
# Functionally complete sets ( AND and NOT gates)



     
# Functionally complete sets ( OR and NOT gates)



# Functionally complete sets (NAND gate)

Desired NOT Gate

 

$$Q = \text{NOT}(A)$$

NAND Construction



$$= A \text{ NAND } A$$

**NOT from NAND**

Truth Table

Input A	Output Q
0	1
1	0

=

A	$Q = \overline{A.A} = \overline{A}$
0	1
1	0


# Functionally complete sets (NAND gate)

Desired AND Gate



$$Q = A \text{ AND } B$$

NAND Construction

 

$$= (A \text{ NAND } B) \text{ NAND } (A \text{ NAND } B)$$

AND from NAND

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

=

A	B	$\overline{A \cdot B}$	$Q = \overline{\overline{A \cdot B}} = A \cdot B$
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1


# Functionally complete sets (NAND gate)

Desired OR Gate



$$Q = A \text{ OR } B$$

NAND Construction

 

$$= (A \text{ NAND } A) \text{ NAND } (B \text{ NAND } B)$$

OR from NAND

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1


=

A	B	$\bar{A}$	$\bar{B}$	$\bar{A} \cdot \bar{B}$	Q
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1



# Functionally complete sets (NOR gate)

Desired NOT Gate

 

$$Q = \text{NOT}(A)$$

NOR Construction



$$= A \text{ NOR } A$$

**NOT from NOR**

Truth Table

Input A	Output Q
0	1
1	0

=

A	$Q = \overline{A + A} = \overline{A}$
0	1
1	0


# Functionally complete sets (NOR gate)

Desired OR Gate



$$Q = A \text{ OR } B$$

NOR Construction

 

$$= (A \text{ NOR } B) \text{ NOR } (A \text{ NOR } B)$$

OR from NOR

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

=

A	B	$\overline{A+B}$	$Q = \overline{\overline{A+B}} = A+B$
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1


# Functionally complete sets (NOR gate)

Desired AND Gate



$$Q = A \text{ AND } B$$

NOR Construction

 

$$= (A \text{ NOR } A) \text{ NOR } (B \text{ NOR } B)$$

AND from NOR

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

=

A	B	$\bar{A}$	$\bar{B}$	$\bar{A} + \bar{B}$	Q
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

# Karnaugh Map (K-Map)

- A gate level minimization technique.
- For a boolean function with  $n$  variables, corresponding K Map have  $2^n$  cells.
- Only one variable changed when moving to an adjacent column or row.

		CD			
		00	01	11	10
A B	00				
	01				
	11				
	10				

	$x = 0$ $y = 0$	$x = 0$ $y = 1$	$x = 1$ $y = 1$	$x = 1$ $y = 0$
$z = 0$				
$z = 1$				

		CDE							
		000	001	011	010	100	101	111	110
A B	00								
	01								
	11								
	10								

5-variable Karnaugh map (overlay)

# Karnaugh Map (K-Map)

- Steps
  1. Mapping
  2. Grouping
  3. Deriving

# K Map - (1) Mapping

- Draw the grid
  - Cells =  $2^n$
- Put 1 to the described terms ; others 0.

# K Map - (1) Mapping

Sum of Minterms

- **Example :**

$$F = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.\bar{z} + x.y.\bar{z}$$

		$\bar{x}\bar{y}$	$\bar{x}y$	$xy$	$x\bar{y}$
$z$	$xy$	00	01	11	10
	$\bar{z}$	0			
	$z$	1			

# K Map - (1) Mapping

- **Example :**

$$F = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.\bar{z} + x.y.\bar{z}$$

		$\bar{x}\bar{y}$	$\bar{x}y$	$xy$	$x\bar{y}$
$\bar{z}$	$z$	00	01	11	10
	0	0	0	1	1
$z$	1	1	1	0	0



# K Map - (2) Grouping

- **Group 1s (For Sum of Products) or 0s (For Product of Sums)**
  - **Grouping can be done vertically or horizontally (Not diagonal).**
  - **Number of cells in a group should be a power of 2 (1,2,4,8 etc.)**
  - **Select the largest group possible.**
  - **Groups can be overlapped to form the largest group.**
  - **Groups can be formed by wrapping around the grid.**
  - **There should be as few groups as possible while covering all the 1s (or 0s).**

# K Map - (2) Grouping

Example :

$$F = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.\bar{z} + x.y.\bar{z}$$

		$\bar{x}\bar{y}$	$\bar{x}y$	$xy$	$x\bar{y}$
		00	01	11	10
$\bar{z}$	$xy$ z	0	0	1	1
$z$		1	1	0	0

# K Map - (3) Deriving

- Write the unchanged terms in each group

# K Map - (3) Deriving

- Group 1 {Red}
- Unchanged:  $x$  and  $\bar{z}$

Example :

$$F = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.\bar{z} + x.y.\bar{z}$$

		$\bar{x}\bar{y}$	$\bar{x}y$	$xy$	$x\bar{y}$
		00	01	11	10
$\bar{z}$	$z$ \ $xy$	0	0	1	1
$z$		1	1	0	0

←  $x.\bar{z}$

# K Map - (3) Deriving

- Group 2 (Blue)
- Unchanged:  $\bar{x}$  and  $z$

Example :

$$F = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.\bar{z} + x.y.\bar{z}$$

		$\bar{x}\bar{y}$	$\bar{x}y$	$xy$	$x\bar{y}$
		00	01	11	10
$\bar{z}$	0	0	0	1	1
$z$	1	1	1	0	0

Diagram illustrating the Karnaugh Map (K Map) for the function  $F$ . The map is a 2x4 grid with columns labeled  $\bar{x}\bar{y}$ ,  $\bar{x}y$ ,  $xy$ , and  $x\bar{y}$ , and rows labeled  $\bar{z}$  and  $z$ . The cells contain values 0 or 1. Two groups are highlighted:

- Group 1 (Red):** A group of two cells in the  $\bar{z}$  row, specifically the cells for  $xy$  and  $x\bar{y}$  (both containing 1). This group is labeled  $x.\bar{z}$ .
- Group 2 (Blue):** A group of two cells in the  $z$  row, specifically the cells for  $\bar{x}\bar{y}$  and  $\bar{x}y$  (both containing 1). This group is labeled  $\bar{x}.z$ .

# K- Map Example

- $F = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C$

# K- Map Example

- $F = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C$

		$\bar{A} \bar{B}$	$\bar{A} B$	$A B$	$A \bar{B}$
$\bar{C}$ $C$	$AB$ $C$	00	01	11	10
	0	1	0	0	0
	1	1	0	0	0

$\bar{A} \bar{B}$

$$A B \bar{C} + \bar{A} \bar{B} C = \bar{A} \bar{B}$$

# K- Map Examples


- $F = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B C + \overline{A} B \overline{C}$



# K- Map Examples

- $F = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} B C + \bar{A} B \bar{C}$

		$\bar{A} \bar{B}$	$\bar{A} B$	$A B$	$A \bar{B}$
		00	01	11	10
$\bar{C}$	0	1	1	0	0
$C$	1	1	1	0	0

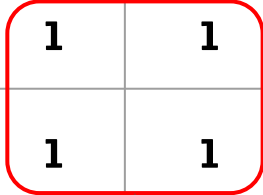
 $\bar{A}$

$$\bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} B C + \bar{A} B \bar{C} = \bar{A}$$

# Exercise

## 1. Simplify using K Maps and validate the result using boolean algebra

- a.  $A'B + AB' + AB$
- b.  $A'BC' + A'BC + A'B'C + ABC$
- c.  $BC + BC' + BA$
- d.  $AB + A(B+C) + B(B+C)$
- e.  $AB' + A(B+C)' + B(B+C)'$